

Circuit - a representation of energy  
gives - (active elements) and energy takers



(passive elements) that for a closed path through which  
current can flow.

Can be represented schematically and mathematically  
\* assumption - Ideal world.

↳ active elements - provide energy
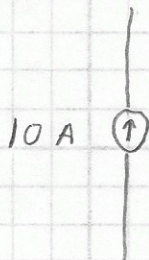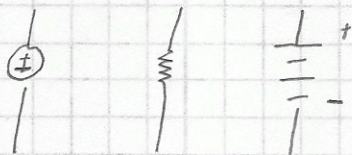
### a. Independent Sources

i voltage source - the value of the voltage between  
the terminals is known; the amount of current  
provided is determined by what it is connected to.




\* There is a voltage  
Associated with  
current sources!


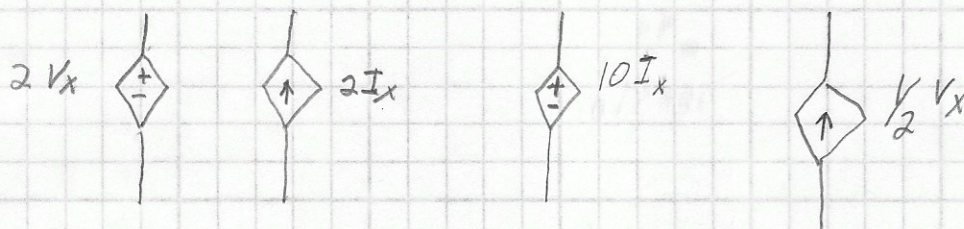
## b. Dependent Sources (controlled sources)

- can be a voltage or current sources
- can depend on a voltage or current else where in the circuit




\* Will need one extra (constraint) eqn.

## 2. Passive Elements

### a. Resistors


- symbol in signs  $R$

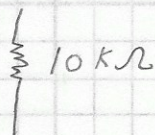

- Units are Ohms ( $\Omega$ )

### b. Capacitors

- symbol in eqns,  $C$

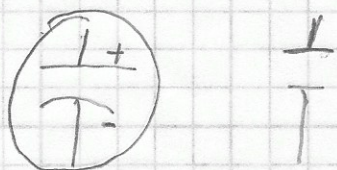

- Units are Farads ( $F$ )



## c. Inductors

- symbol in eqns,  $L$




- Units are Henrys (H)
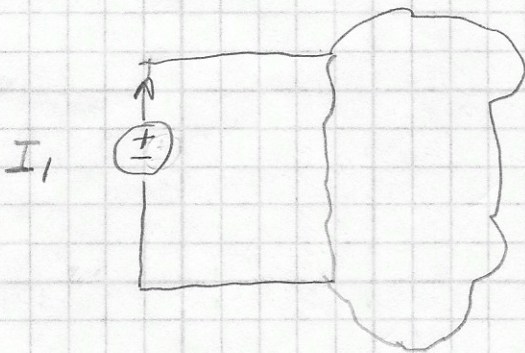
### Current

- symbol in eqns is  $i$   $\swarrow$  time dependent (AC) or  $I$   $\swarrow$  constant (DC)

- Defined based on direction positive charges would flow.



Current is the rate of flow of charges

$$1 \text{ Ampere} = 1 \text{ C/s}$$

$$A = 1 \text{ C/s}$$

(Amps) A

- If current enters an element at the point of highest voltage and leaves at the point of lowest voltage, that element is passive


### Voltage

- better term  $\Rightarrow$  potential difference
- Voltage is the difference in electric potential energy (per unit of charge) between two points

$$1 \text{ volt} = 1 \text{ V/C}$$



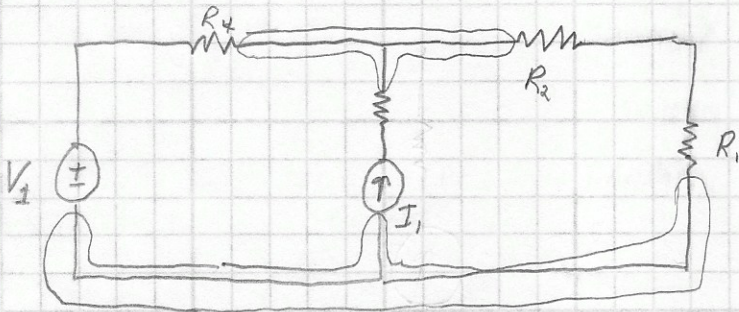The voltage (potential difference) between two points in a circuit is independent of the path taken between those points.



node - a point (wires connecting elements) where 3\* or more elements are connected.

• branch - the element(s) that connect two nodes

• mesh - a region of space enclosed by branches


single - Arrow Notation  $10V$



3-0235 — 50 SHEETS — 5 SQUARES  
 3-0236 — 100 SHEETS — 5 SQUARES  
 3-0237 — 200 SHEETS — 5 SQUARES  
 3-0137 — 200 SHEETS — FILLER

COMET


Ex:

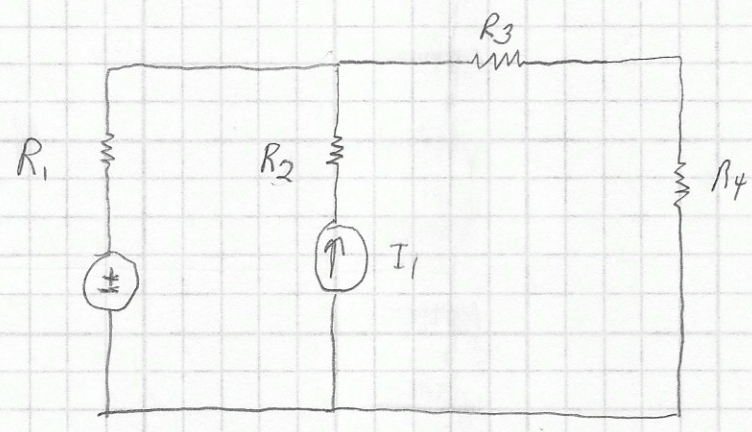

series - elements that are connected "end-to-end"  
 The only node between them is a connection of only 2 elements

\* The elements in series share the same current!  
 parallel - elements and branches, that are connected between the same two nodes.

ex:

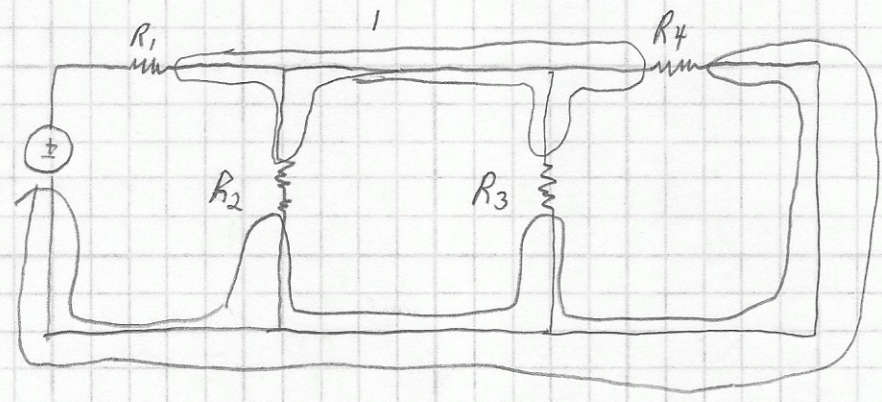


$$R_2 \parallel R_3 \parallel R_4$$

Elements in parallel have the same voltage!



## Fundamental Laws of Circuit Analysis

① Ohm's Law  $V = IR$

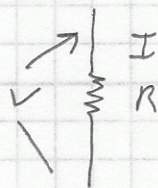

② Kirchhoff's Current Law (KCL)

The total current entering a node must be equal to the total current leaving the node.

$$\sum I_{in} = \sum I_{out}$$

③ Kirchhoff's Voltage Law (KVL)

Around any complete loop (starting & finishing at the same node), the total change in voltage must equal zero.

\*  $\sum V = 0$  around closed loop.


$$\sum V_{rise} = \sum V_{drop}$$

4. Power Law

$$P = IV \quad (= I^2 R = V^2 / R)$$

$$= (C/s)(J/C) = J/s = W$$
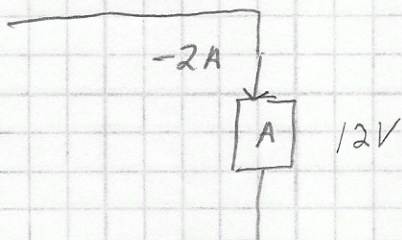
$$\sum P_{supplied} = \sum P_{absorbed} \text{ for the whole circuit}$$






## Additional Tools

### ① Equivalent Resistance

#### Resistors in Series

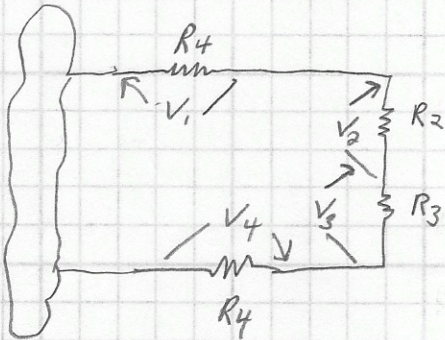


$$\begin{aligned}
 V_{tot} &= V_1 + V_2 + V_3 + V_4 \\
 &= IR_1 + IR_2 + IR_3 + IR_4 \\
 &= I (R_1 + R_2 + R_3 + R_4)
 \end{aligned}$$

$$V_{tot} = I R_{eq}$$

$$R_{eq} = \sum R_i$$

#### Resistor in Parallel

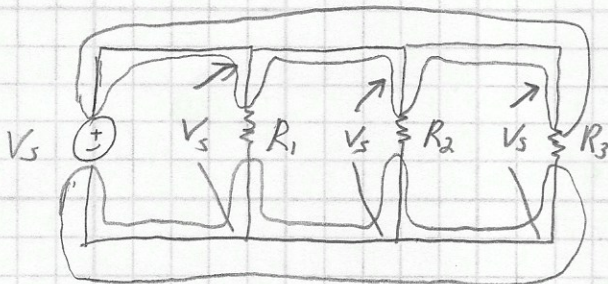



KCL:  $I_s = I_1 + I_2 + I_3$



$$I_s = \frac{V_s}{R_1} + \frac{V_s}{R_2} + \frac{V_s}{R_2}$$

$$I_s = V_s \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\left( \frac{1}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} \right) I_s = V_s$$

$$R_{eq} I_s = V_s$$
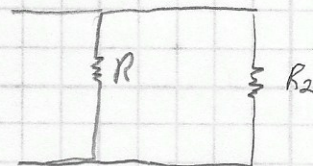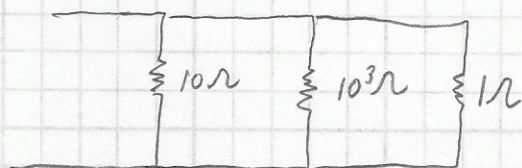
$$\frac{1}{R_{eq}} = \sum \frac{1}{R_i}$$



$$\frac{1}{R_{eq}} = \frac{R_2}{R_2 R_1} + \frac{R_1}{R_2 R_1}$$


$$\frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{\text{product}}{\text{sum}}$$



## 2. Voltage Division

- Only works w/ resistor in series!

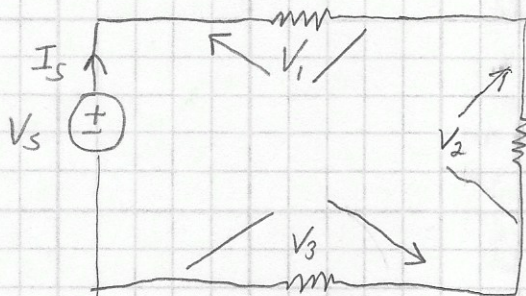


$$\frac{V_2}{V_s} = \frac{I_s R_2}{I_s R_{eq}} = \frac{I_s R_2}{I_s (R_1 + R_2 + R_3)}$$

$$V_2 = \frac{R_2}{R_{eq}} V$$

$$V_i = \boxed{\frac{R_i}{R_{eq}} V_s}$$

## 3. Current Division

Only works with resistors in parallel!

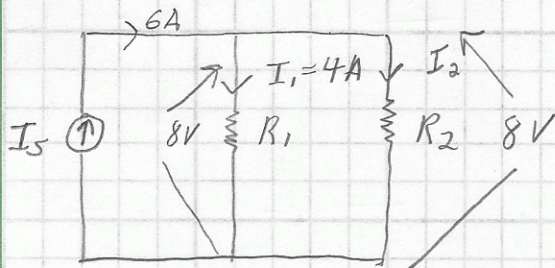

$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) I_s$$

Annotations for the formula above:

- Opposite branch (points to  $R_1$  in the numerator)
- sum of R's (points to  $R_1 + R_2$  in the denominator)
- current that is dividing (points to  $I_s$ )



$$I_2 = \left( \frac{2\Omega}{2\Omega + 4\Omega} \right) (6A) = 2A$$

sum of R's

\*  $\rightarrow$  current travels through the path of least resistance.

\* Any time you have a controlled source there is one extra equation